

E E 476 – Introduction to VLSI Design
Mid-term examination
November 4th, 2022

I have not received nor obtained help from anyone in the completion of this examination. During the course of this mid-term examination, I have not engaged with any form of communication with my peers on any aspect of the contents of this exam. I understand that strict action will be taken resulting from my failure to comply with the mid-term examination policy. I also understand that it is my duty to not only adhere to the mid-term exam policy, but also report any other individual(s) who are violating this policy.

Name: _____

Signature: _____

The use of notes, calculators, or any electronic devices is not allowed during this midterm examination.

Duration: 50 minutes

Assume that all devices have 0 leakage current. Unless otherwise stated, the following default parameters apply:

| | | |
|------------------------------------|----------------------------------------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| V_{dd} | 1.2 V | $C_{ox} = \frac{\epsilon_r \cdot \epsilon_0}{t_{ox}} = 0.01 \text{ F/m}^2$ $\mu_n \cdot C_{ox} = 0.5 \text{ mA}$ $\mu_p \cdot C_{ox} = 0.25 \text{ mA}$ $\mu_n \cdot C_{ox} \cdot \frac{W_n}{L} = 10 \text{ mA}$ $\mu_p \cdot C_{ox} \cdot \frac{W_p}{L} = 10 \text{ mA}$ |
| ϵ_r (Silicon-di-oxide) | 3.8 | |
| ϵ_0 | $8.85 \cdot 10^{-12} \text{ F/m}$ | |
| λ | 0 | |
| t_{ox} | $33.63 \text{ \AA} = 3.363 \text{ nm}$ | |
| μ_n | $500 \text{ cm}^2/\text{V}$ | |
| μ_p | $250 \text{ cm}^2/\text{V}$ | |
| $V_{th,n} = V_{th,p} = V_{th}$ | 0.2 V | |
| W_n | 1 μm | |
| W_p | 2 μm | |
| Beta ratio = $\frac{\mu_n}{\mu_p}$ | 2 | |
| $L_n = L_p = L$ | 50 nm | |


NMOS transistor:

| | | |
|---------------|--------------------------------------------------------|---------------------------------------------------------------------------------------------------------------------|
| Cut-off | $V_{GS} \leq V_{th}$ | $I_D = 0$ |
| Linear/Triode | $V_{GS} > V_{th}$ and $V_{DS} \leq V_{GS} - V_{th}$ | $I_D = \mu_n \cdot C_{ox} \cdot \frac{W_n}{L} \left[(V_{GS} - V_{th}) \cdot V_{DS} - \frac{1}{2} V_{DS}^2 \right]$ |
| Saturation | $V_{GS} > V_{th}$ and $V_{DS} > V_{GS} - V_{th}$ | $I_D = \frac{1}{2} \cdot \mu_n \cdot C_{ox} \cdot \frac{W_n}{L} (V_{GS} - V_{th})^2 (1 + \lambda \cdot V_{DS})$ |



PMOS transistor:

| | | |
|---------------|--------------------------------------------------------|---------------------------------------------------------------------------------------------------------------------|
| Cut-off | $V_{SG} \leq V_{th}$ | $I_D = 0$ |
| Linear/Triode | $V_{SG} > V_{th}$ and $V_{SD} \leq V_{SG} - V_{th}$ | $I_D = \mu_p \cdot C_{ox} \cdot \frac{W_p}{L} \left[(V_{SG} - V_{th}) \cdot V_{SD} - \frac{1}{2} V_{SD}^2 \right]$ |
| Saturation | $V_{SG} > V_{th}$ and $V_{SD} > V_{SG} - V_{th}$ | $I_D = \frac{1}{2} \cdot \mu_p \cdot C_{ox} \cdot \frac{W_p}{L} (V_{SG} - V_{th})^2 (1 + \lambda \cdot V_{SD})$ |

 
- 1 .- **(5 points)** Consider the inverter in the figure to the right, where $C_L = 100$ fF. Is it true that we can make the propagation delay of this gate as small as we want by increasing W ? Why or why not?



  - 2 .- **(5 points)** Which of the following circuits is an acceptable implementation of CMOS logic? Why?



 
3.- (5 points) Consider the figure to the right, where the two inverters are identical. τ_1 and τ_2 are the propagation times for each inverter. Similarly, E_1 and E_2 are the energies consumed by each inverter when their input transitions twice, as shown with the blue waveform.




a) Are the two delays equal? If not, which is greater, τ_1 or τ_2 ?

b) If we assume that the inverters don't have any parasitic capacitance, what is the value of the ratio $\frac{E_2}{E_1}$?


 
4.- (5 points) Which of the following two layouts of a NAND gate takes advantage of "drain sharing"?



 
- 5 .- **(5 points)** Consider the following voltage-transfer curves for two separate inverters. Based on the curves, which inverter is more immune to noise in the input? Why?



  
- 6 .- **(10 points)** The figure below shows an inverter, and a sketch of its DC voltage transfer characteristic. What is the value of V_T ?



 - 6 .- **(15 points)** Draw the transistor-level schematic that corresponds to the stick diagram in the figure below
- (BONUS: 5 points)** What is the function of this circuit?



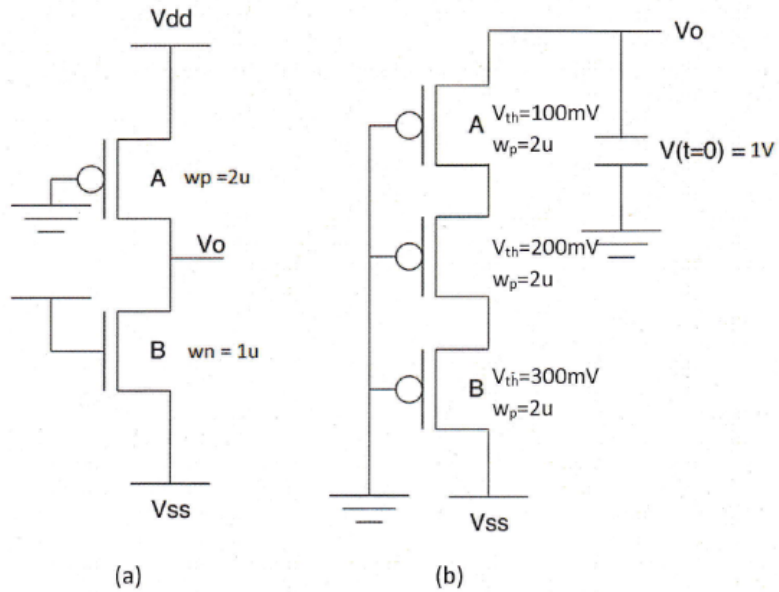7 .- **(10 points)** For the given circuits in the figure below, (a) and (b), find V_o and the state in which devices A and B are (linear/saturation/cutoff). Assume no leakage in the transistors. Fill up Table 1 to indicate your answers, and briefly explain how you deduced them.



| | V_o | State of device A | State of device B |
|-----|-------|-------------------|-------------------|
| (a) | | | |
| (b) | | | |