

# Lecture 6: Gate Delay



*Based on material prepared by prof. Visvesh S. Sathe*

# Acknowledgements


All class materials (lectures, assignments, etc.) based on material prepared by Prof. Visvesh S. Sathe, and reproduced with his permission



Visvesh S. Sathe  
Associate Professor  
Georgia Institute of Technology  
<https://psylab.ece.gatech.edu>

UW (2013-2022)  
GaTech (2022-present)


# CMOS Inverter Delay

 

## ■ Definitions:


- Rise delay - Input 50% fall to output 50% rise
- Fall delay - Input 50% rise to output 50% fall
- Rise time – Output 20% rise to 80% rise
- Fall time – Output 80% fall to 20% fall

# Simple Delay Model

 


- Gate delays determine the time taken to compute a boolean function

# Simple Delay Model

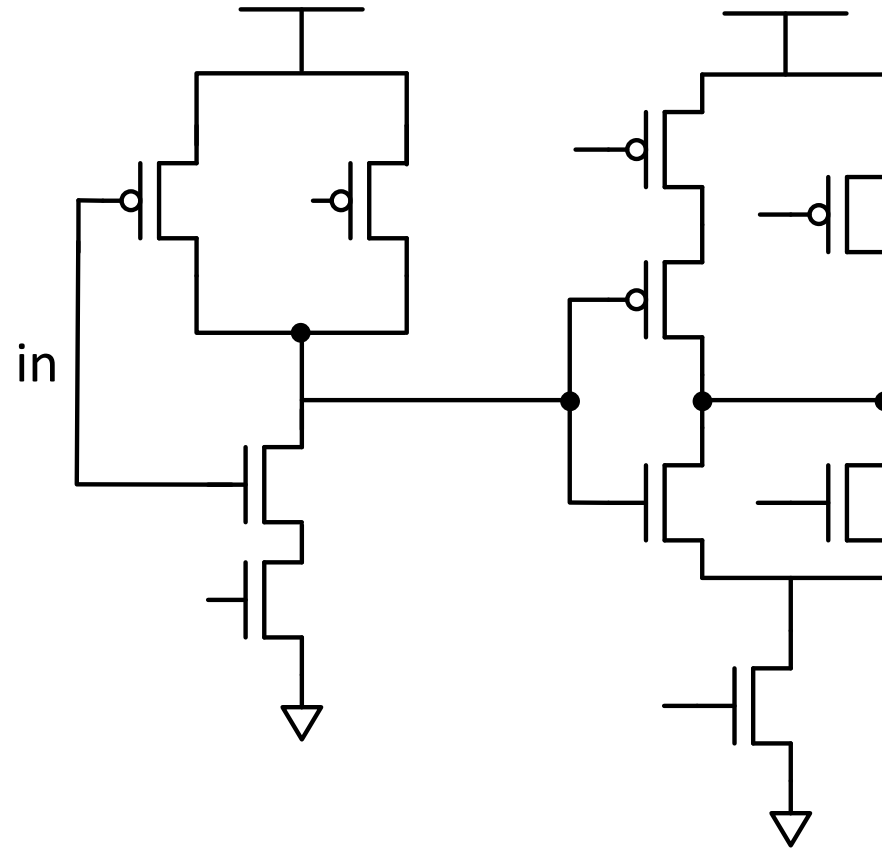


- Pmos or Nmos device drive capacitive load to charge (discharge) output to logic 1 (0)

# Simple Delay Model

 


- Pmos or Nmos device drive capacitive load to charge (discharge) output to logic 1 (0)

# Simple Delay Model

 

- Pmos or Nmos device drive capacitive load to charge (discharge) output to logic 1 (0)


# Simple Delay Model

 

- Pmos or Nmos device drive capacitive load to charge (discharge) output to logic 1 (0)




# Simple Delay Model

 


- Pmos or Nmos device drive capacitive load to charge (discharge) output to logic 1 (0)

# Simple Delay Model

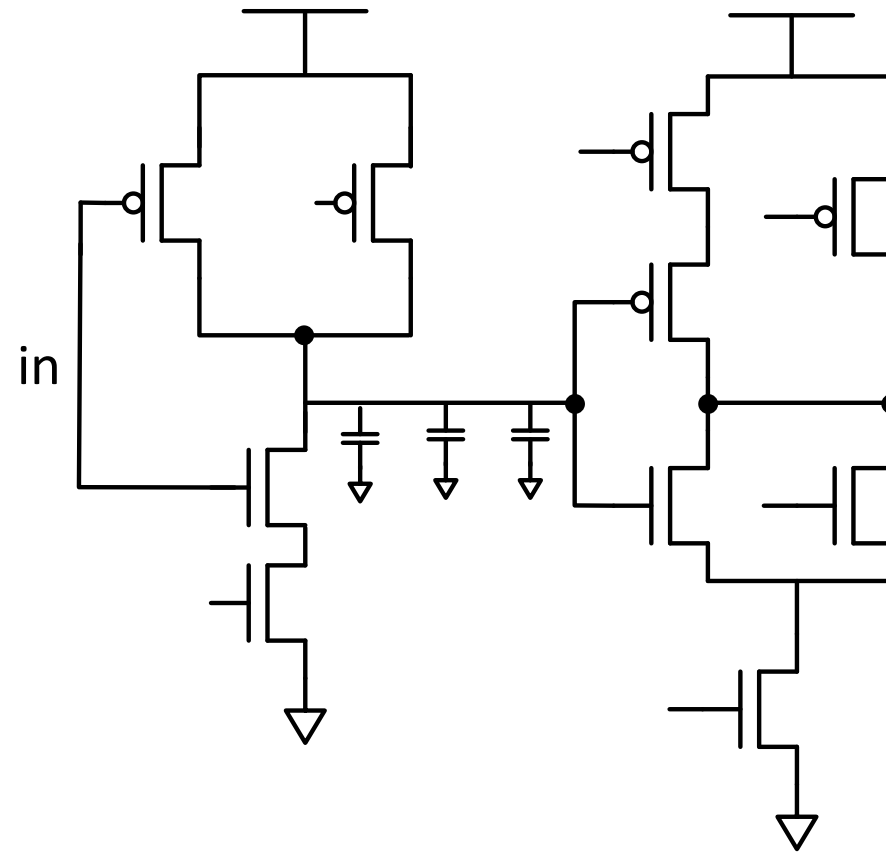


- Effectively 3 components

# Simple Delay Model

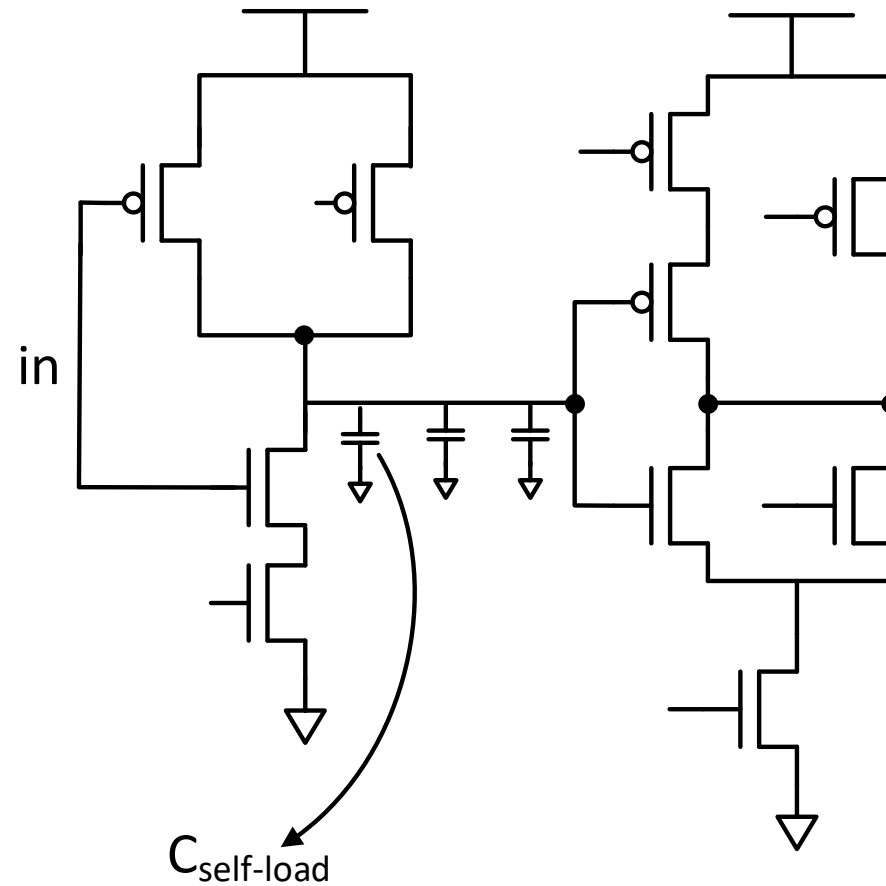


- Effectively 3 components

# Simple Delay Model

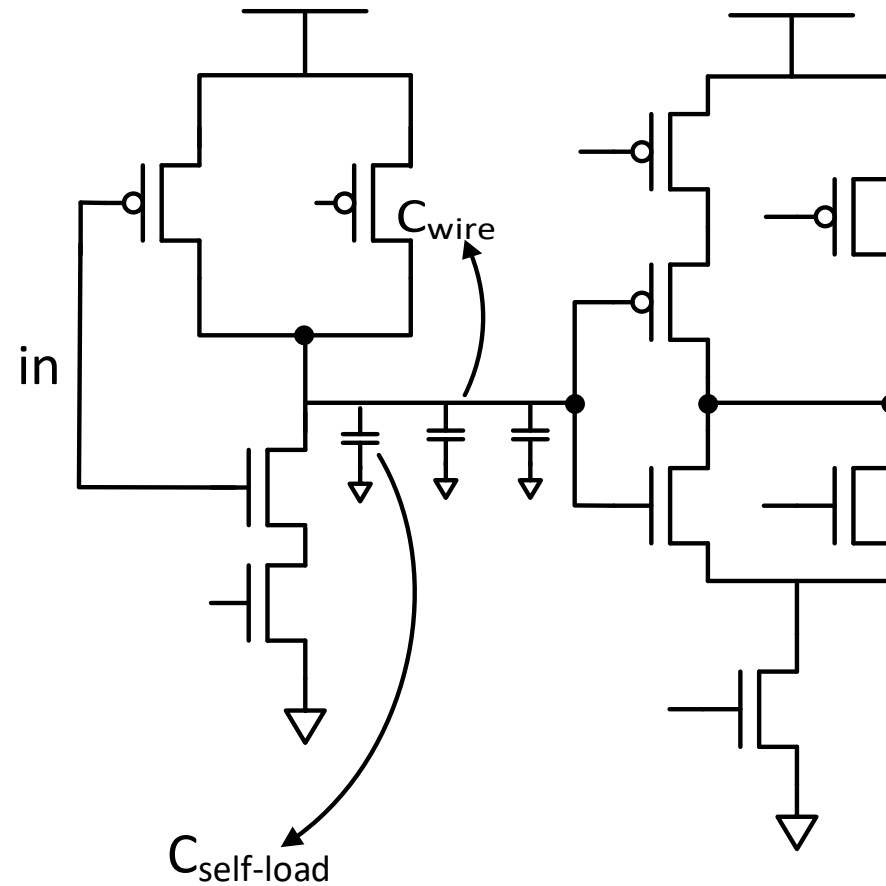



- Effectively 3 components

# Simple Delay Model

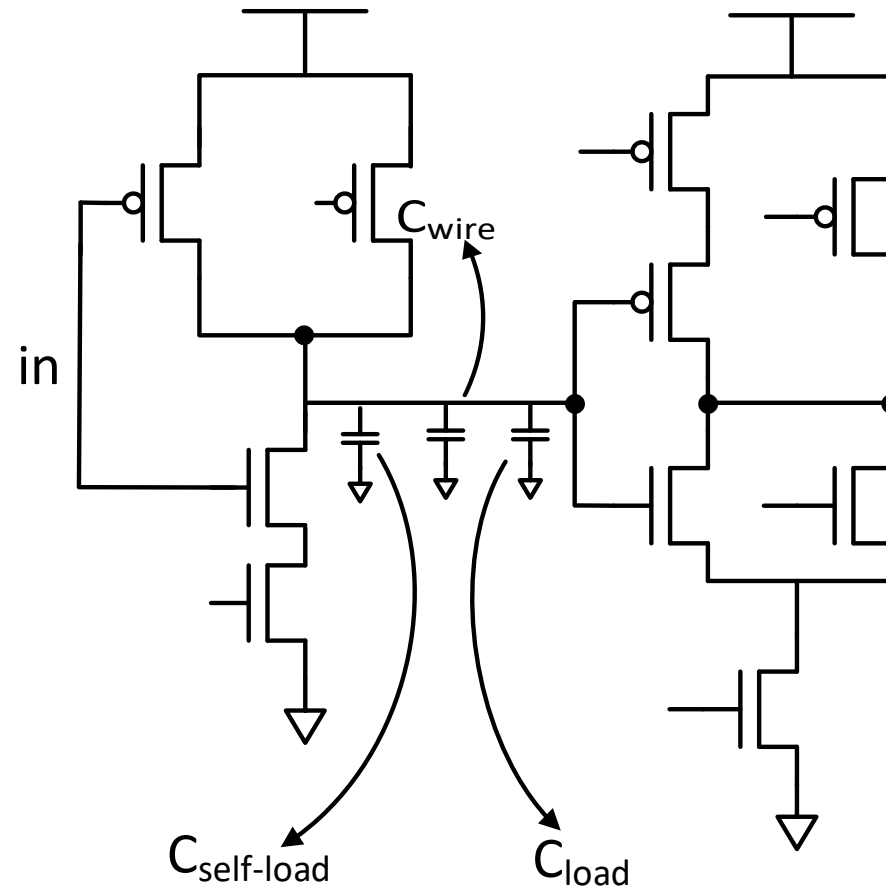


- Effectively 3 components

# Simple Delay Model

  


- Circuit delay viewed as
  - Voltage-dependent current source charging/discharging capacitance
  - Voltage-dependent resistance charging/discharging capacitance

# Charging/Discharging Current

 

- Gate evaluating to Vdd
  - PMOS operating in different regions
  - Working out exact equations is not productive
  - Design perspective: Linear or Saturation, current drive scaled by  $W$ ,  $1/L$

# Delay Dependence on W

 

- Does delay scale as  $1/W$ ?




# Delay Dependence on W



If I have 2 cascaded inverters and the scale,  $x$  of the driving inverter is variable, how does the delay vary with  $x$

- Does delay scale as  $1/W$ ?

# Delay Dependence on W

 


Self-loading!

- Does delay scale as  $1/W$ ?



If I have 2 cascaded inverters and the scale,  $x$  of the driving inverter is variable, how does the delay vary with  $x$

# Delay Dependence on L

 


Delay vs. L\_factor

Delay (ps)


L\_factor

- If W and L are both designer tunable, why do most digital designs tweak only W?

# Delay Dependence on L

 


Delay vs. L\_factor

 

- If W and L are both designer tunable, why do most digital designs tweak only W?

# Delay Dependence on L

 


Delay vs. L\_factor

Delay (ps)

L\_factor

- If W and L are both designer tunable, why do most digital designs tweak only W?

# Delay Dependence on L

 

Delay vs. L\_factor



Delay (ps)

L\_factor

Extra:  
Relationship with  
L is Linear (Affine, y-intercept)

- If W and L are both designer tunable, why do most digital designs tweak only W?

# Delay Dependence on C

  

- Self loading causes non-zero intercept

# Delay Dependence on $V_{dd}$

---




# Delay Dependence on Vdd

- $\uparrow V_{dd} \rightarrow \downarrow \text{Delay}$

# Delay Dependence on Vdd


- $\uparrow V_{dd} \rightarrow \downarrow \text{Delay}$
- $\tau = \frac{Q_{load}}{I} = \frac{C_{load}V_{dd}}{I} = \frac{kC_{load}V_{dd}}{\beta (V_{dd}-V_{th})^\alpha}$

# Delay Dependence on Vdd

 


- $\uparrow V_{dd} \rightarrow \downarrow \text{Delay}$
- $$\tau = \frac{Q_{load}}{I} = \frac{C_{load}V_{dd}}{I} = \frac{kC_{load}V_{dd}}{\beta (V_{dd}-V_{th})^\alpha}$$

# Delay Dependence on Vdd

 


- $\uparrow V_{dd} \rightarrow \downarrow \text{Delay}$

 - $$\tau = \frac{Q_{load}}{I} = \frac{C_{load}V_{dd}}{I} = \frac{kC_{load}V_{dd}}{\beta (V_{dd}-V_{th})^\alpha}$$




# CMOS Inverter Delay : Inverter model

 

- Simplified views:
  - Effective resistance
  - Notice  $2W$  allows twice the current (half the resistance)
  - $2L$  allows half the current
  - Limitations (small signal resistance is diff.)
- Can also think of equivalent current source?
  - Current source a function of  $V_{gs}$ ,  $V_{th}$ ,  $W$ ,  $L$  (No control over  $V_{th}^*$ ,  $\mu$ ,  $C_{ox}$ )
  - Norton resistance for  $\lambda$
  - Typically device operates in saturation while bringing output to 50%

# CMOS Inverter Delay : Inverter model

 

Estimate  $R(V)$

$I_{\text{eff}}(V)$

- Simplified views:
  - Effective resistance
  - Notice  $2W$  allows twice the current (half the resistance)
  - $2L$  allows half the current
  - Limitations (small signal resistance is diff.)
- Can also think of equivalent current source?
  - Current source a function of  $V_{\text{gs}}, V_{\text{th}}, W, L$  (No control over  $V_{\text{th}}^*, \mu, C_{\text{ox}}$ )
  - Norton resistance for  $\lambda$
  - Typically device operates in saturation while bringing output to 50%

# Delay analysis : Some Thoughts


- Designers casually refer to the “resistance of the inverter”
  - If this resistance is a constant, what will be the impact of voltage on delay with the RC model?
- Scaled technologies rely on  $\uparrow C_{ox}$  for improved current drive...
  - But what's the point if that increases the load of the transistor?!

# Delay analysis : Some Thoughts

- Designers casually refer to the “resistance of the inverter”
  - If this resistance is a constant, what will be the impact of voltage on delay with the RC model?
  - Resistance is Voltage Dependent!
- Scaled technologies rely on  $\uparrow C_{ox}$  for improved current drive...
  - But what's the point if that increases the load of the transistor?!




# CMOS Gate Delay : Input Ordering

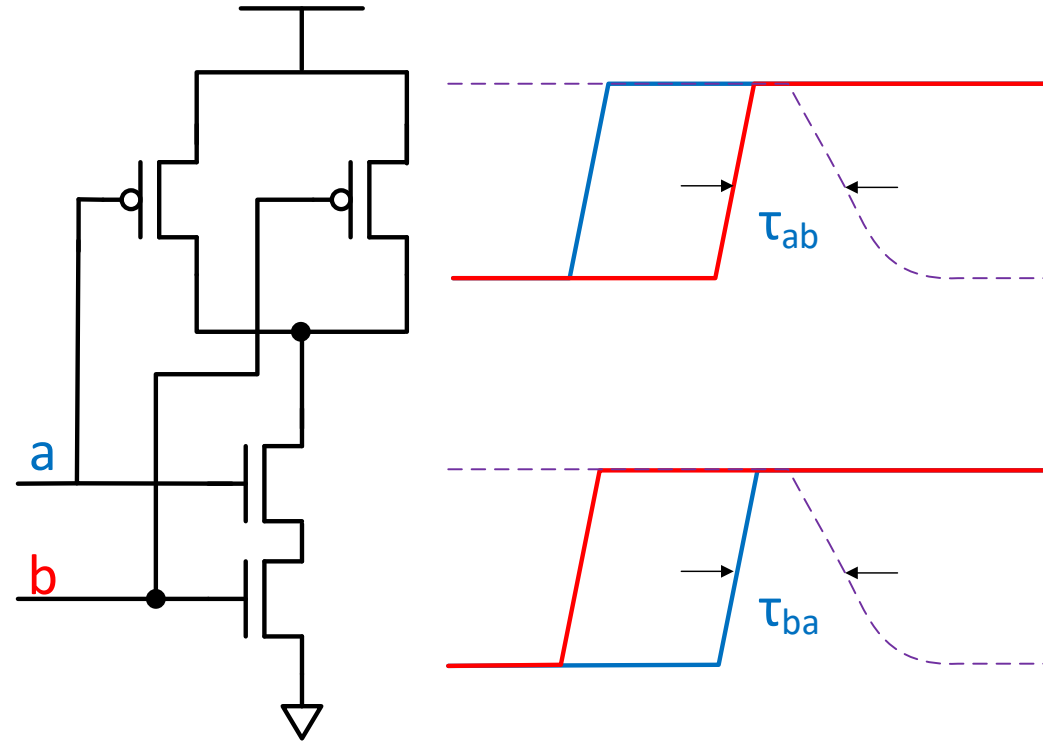


- Which is faster?  $\tau_{ba}$  or  $\tau_{ab}$  ??

# Inverter Chain

 

- Total delay =  $\sum \tau_i$
- How can we achieve minimum delay?

# Inverter Chain

 

- In general, given a chain with:
  - Fixed input cap
  - Output load

# Inverter Chain (contd)

- Assume balanced rise/fall delay
- $\tau = \sum \tau_i = \sum R_i C_{i+1}$
- $R = k/C$
- $\tau = R_0 C_1 + R_1 C_{out}$

$$\begin{aligned} &= \frac{kC_1}{C_0} + \frac{kC_{out}}{C_1} \\ &= k \left( \frac{C_1}{C_0} + \frac{C_{out}}{C_1} \right) \end{aligned}$$

- Setting  $\frac{\partial \tau}{\partial C_1} = 0$  gives ...


# Inverter Chain (contd)

- Assume balanced rise/fall delay
- $\tau = \sum \tau_i = \sum R_i C_{i+1}$
- $R = k/C$
- $\tau = R_0 C_1 + R_1 C_{out}$

$$\begin{aligned} &= \frac{kC_1}{C_0} + \frac{kC_{out}}{C_1} \\ &= k \left( \frac{C_1}{C_0} + \frac{C_{out}}{C_1} \right) \end{aligned}$$


- Setting  $\frac{\partial \tau}{\partial C_1} = 0$  gives ...
- $C_1 = k\sqrt{C_0 C_{out}}$
- $\tau_{min} = 2k\sqrt{C_{out}/C_0}$

# Intrinsic RC delay

 

$$\begin{aligned} R &= k_r / W_n \\ C &= k'_c (W_n + W_p) \\ &= k'_c W_n (1 + \beta) \\ &= k_c W_n \end{aligned}$$

 
$$\begin{aligned} R_n &= \\ C_{in} &= \\ R_n C_{in} &= \end{aligned}$$



$$\begin{aligned} R_n &= \\ C_{in} &= \\ R_n C_{in} &= \end{aligned}$$


- Not to be confused with self loading
- $R_{\text{eff}} C_{\text{in}}$  product of an inverter (assume balanced inverter)
  - Independent of sizing
  - Topology driven
- Quick exercise: Compute  $R_n C_n$  for a 2 input NOR
  - Repeat  $R_p C_{\text{in}}$  calculation assuming  $\beta=3.5$

# Intrinsic RC delay

 

$$\begin{aligned} R &= k_r / W_n \\ C &= k'_c (W_n + W_p) \\ &= k'_c W_n (1 + \beta) \\ &= k_c W_n \end{aligned}$$

 
$$\begin{aligned} R_n &= \frac{k_r}{1.0} \\ C_{in} &= \\ R_n C_{in} &= \end{aligned}$$



$$\begin{aligned} R_n &= \\ C_{in} &= \\ R_n C_{in} &= \end{aligned}$$


- Not to be confused with self loading
- $R_{\text{eff}} C_{\text{in}}$  product of an inverter (assume balanced inverter)
  - Independent of sizing
  - Topology driven
- Quick exercise: Compute  $R_n C_n$  for a 2 input NOR
  - Repeat  $R_p C_{\text{in}}$  calculation assuming  $\beta=3.5$

# Intrinsic RC delay

 

$$\begin{aligned} R &= k_r / W_n \\ C &= k'_c (W_n + W_p) \\ &= k'_c W_n (1 + \beta) \\ &= k_c W_n \end{aligned}$$
 
$$\begin{aligned} R_n &= \frac{k_r}{1.0} \\ C_{in} &= 3.5 k'_c \\ R_n C_{in} &= \end{aligned}$$




$$\begin{aligned} R_n &= \\ C_{in} &= \\ R_n C_{in} &= \end{aligned}$$

- Not to be confused with self loading
- $R_{\text{eff}} C_{\text{in}}$  product of an inverter (assume balanced inverter)
  - Independent of sizing
  - Topology driven
- Quick exercise: Compute  $R_n C_n$  for a 2 input NOR
  - Repeat  $R_p C_{\text{in}}$  calculation assuming  $\beta=3.5$




# Intrinsic RC delay

 

$$\begin{aligned} R &= k_r / W_n \\ C &= k'_c (W_n + W_p) \\ &= k'_c W_n (1 + \beta) \\ &= k_c W_n \end{aligned}$$

 
$$\begin{aligned} R_n &= \frac{k_r}{1.0} \\ C_{in} &= 3.5k'_c \\ R_n C_{in} &= 3.5k_r k'_c \end{aligned}$$



$$\begin{aligned} R_n &= \\ C_{in} &= \\ R_n C_{in} &= \end{aligned}$$


- Not to be confused with self loading
- $R_{\text{eff}} C_{\text{in}}$  product of an inverter (assume balanced inverter)
  - Independent of sizing
  - Topology driven
- Quick exercise: Compute  $R_n C_n$  for a 2 input NOR
  - Repeat  $R_p C_{\text{in}}$  calculation assuming  $\beta=3.5$

# Intrinsic RC delay

 

$$\begin{aligned} R &= k_r / W_n \\ C &= k'_c (W_n + W_p) \\ &= k'_c W_n (1 + \beta) \\ &= k_c W_n \end{aligned}$$

 
$$\begin{aligned} R_n &= \frac{k_r}{1.0} \\ C_{in} &= 3.5 k'_c \\ R_n C_{in} &= 3.5 k_r k'_c \end{aligned}$$



$$\begin{aligned} R_n &= \frac{k_r}{2.0} \\ C_{in} &= \\ R_n C_{in} &= \end{aligned}$$


- Not to be confused with self loading
- $R_{\text{eff}} C_{\text{in}}$  product of an inverter (assume balanced inverter)
  - Independent of sizing
  - Topology driven
- Quick exercise: Compute  $R_n C_n$  for a 2 input NOR
  - Repeat  $R_p C_{\text{in}}$  calculation assuming  $\beta=3.5$

# Intrinsic RC delay

 

$$\begin{aligned} R &= k_r / W_n \\ C &= k'_c (W_n + W_p) \\ &= k'_c W_n (1 + \beta) \\ &= k_c W_n \end{aligned}$$

 
$$\begin{aligned} R_n &= \frac{k_r}{1.0} \\ C_{in} &= 3.5 k'_c \\ R_n C_{in} &= 3.5 k_r k'_c \end{aligned}$$



$$\begin{aligned} R_n &= \frac{k_r}{2.0} \\ C_{in} &= k'_c \times 7.0 \\ R_n C_{in} &= \end{aligned}$$


- Not to be confused with self loading
- $R_{\text{eff}} C_{\text{in}}$  product of an inverter (assume balanced inverter)
  - Independent of sizing
  - Topology driven
- Quick exercise: Compute  $R_n C_n$  for a 2 input NOR
  - Repeat  $R_p C_{\text{in}}$  calculation assuming  $\beta=3.5$

# Intrinsic RC delay

 

$$\begin{aligned} R &= k_r / W_n \\ C &= k'_c (W_n + W_p) \\ &= k'_c W_n (1 + \beta) \\ &= k_c W_n \end{aligned}$$

 
$$\begin{aligned} R_n &= \frac{k_r}{1.0} \\ C_{in} &= 3.5k'_c \\ R_n C_{in} &= 3.5k_r k'_c \end{aligned}$$



$$\begin{aligned} R_n &= \frac{k_r}{2.0} \\ C_{in} &= k'_c \times 7.0 \\ R_n C_{in} &= 3.5k_r k'_c \end{aligned}$$

- Not to be confused with self loading
- $R_{\text{eff}} C_{\text{in}}$  product of an inverter (assume balanced inverter)
  - Independent of sizing
  - Topology driven
- Quick exercise: Compute  $R_n C_n$  for a 2 input NOR
  - Repeat  $R_p C_{\text{in}}$  calculation assuming  $\beta=3.5$

# A Slightly More General Problem

 


- Solve for optimal  $C_0, C_1 \dots C_{n-1}$  given  $C_n$  and  $C_0$
- Recall  $\tau = \sum \tau_i$

$$\tau = \sum R_i C_{i+1} = \sum \frac{k C_{i+1}}{C_i}$$

- Minimizing multivariate functions

# A Slightly More General Problem

 

- Solve for optimal  $C_0, C_1 \dots C_{n-1}$  given  $C_n$  and  $C_0$
- Recall  $\tau = \sum \tau_i$


$$\tau = \sum R_i C_{i+1} = \sum \frac{k C_{i+1}}{C_i}$$

- Minimizing multivariate functions

What is k again?



# A Slightly More General Problem

 

- Solve for optimal  $C_0, C_1 \dots C_{n-1}$  given  $C_n$  and  $C_0$
- Recall  $\tau = \sum \tau_i$

$$\tau = \sum R_i C_{i+1} = \sum \frac{k C_{i+1}}{C_i}$$

- Minimizing multivariate functions  $\dots \nabla \tau = 0$

What is k again?



# Minimization of $\tau$


- Solving gives  $\frac{C_1}{C_0} = \frac{C_2}{C_1} = \dots \frac{C_{n-1}}{C_{n-2}} = \frac{C_n}{C_{n-1}} = h$
- However,  $\frac{C_n}{C_0} = \text{constant} = \prod \frac{C_{i+1}}{C_i} = \prod h_i$  (Telescoping...)
- Important assumptions
  - All of the input capacitance of the inverter scales with W
    - Wire cap ignored
    - Poly-contact cap ignored
  - Mosfet serves as the only source of resistance
- Question: How does self-loading impact the optimal solution?



# Minimization of $\tau$


- Solving gives  $\frac{C_1}{C_0} = \frac{C_2}{C_1} = \dots \frac{C_{n-1}}{C_{n-2}} = \frac{C_n}{C_{n-1}} = h$
- However,  $\frac{C_n}{C_0} = \text{constant} = \prod \frac{C_{i+1}}{C_i} = \prod h_i$  (Telescoping...)
- $\frac{C_n}{C_0} = h^n \Rightarrow h = \sqrt[n]{\frac{C_n}{C_0}}$
- Important assumptions
  - All of the input capacitance of the inverter scales with W
    - Wire cap ignored
    - Poly-contact cap ignored
  - Mosfet serves as the only source of resistance
- Question: How does self-loading impact the optimal solution?

# Sizing Example

 


- Note:  $C_{in}$  and  $C_{out}$  units are not consistent

# Sizing Example

 


- Note:  $C_{in}$  and  $C_{out}$  units are not consistent
- $C_{in} = 3.5 * 8/7 = 4\text{f}$

# Sizing Example

 


- Note:  $C_{\text{in}}$  and  $C_{\text{out}}$  units are not consistent
- $C_{\text{in}} = 3.5 \cdot 8/7 = 4\text{f}$
- $h^3 = 20/4 \Rightarrow h = \sqrt[3]{5} = 1.71$

# Sizing Example

 


- Note:  $C_{\text{in}}$  and  $C_{\text{out}}$  units are not consistent
- $C_{\text{in}} = 3.5 * 8/7 = 4\text{f}$
- $h^3 = 20/4 \Rightarrow h = \sqrt[3]{5} = 1.71$
- $C_1 = 4\text{f} * 1.71 = 6.84 \Rightarrow W_{p1} = 4.25\mu\text{m}, W_{n1} = 1.71\mu\text{m}$

# Sizing Example

 


- Note:  $C_{\text{in}}$  and  $C_{\text{out}}$  units are not consistent
- $C_{\text{in}} = 3.5 * 8/7 = 4\text{f}$
- $h^3 = 20/4 \Rightarrow h = \sqrt[3]{5} = 1.71$
- $C_1 = 4\text{f} * 1.71 = 6.84 \Rightarrow W_{p1} = 4.25 \mu\text{m}, W_{n1} = 1.71 \mu\text{m}$
- $C_2 = C_1 * 1.71 = 11.69 \Rightarrow W_{p1} = 7.30 \mu\text{m}, W_{n1} = 2.92 \mu\text{m}$

# Practical Sizing Considerations

 


- Better to err on the side of larger drivers
- Min width issues (Allowed/Recommended for technology)
- Technique is great as an **initial starting point** for design
 
## Quick Note on General Sizing (Extra...)




 - $$\tau = \sum \tau_i = \sum R_i C_{i+1} = \sum R_i C_i \frac{C_{i+1}}{C_i}$$
$$= \sum \tau_{intrinsic} \frac{C_{i+1}}{C_i}$$





 
# Quick Note on General Sizing (Extra...)




- $$\tau = \sum \tau_i = \sum R_i C_{i+1} = \sum R_i C_i \frac{C_{i+1}}{C_i}$$

 
$$= \sum \tau_{intrinsic} \frac{C_{i+1}}{C_i}$$
- $$RC_{intrinsic,inv} = 3.5k_r k_c$$



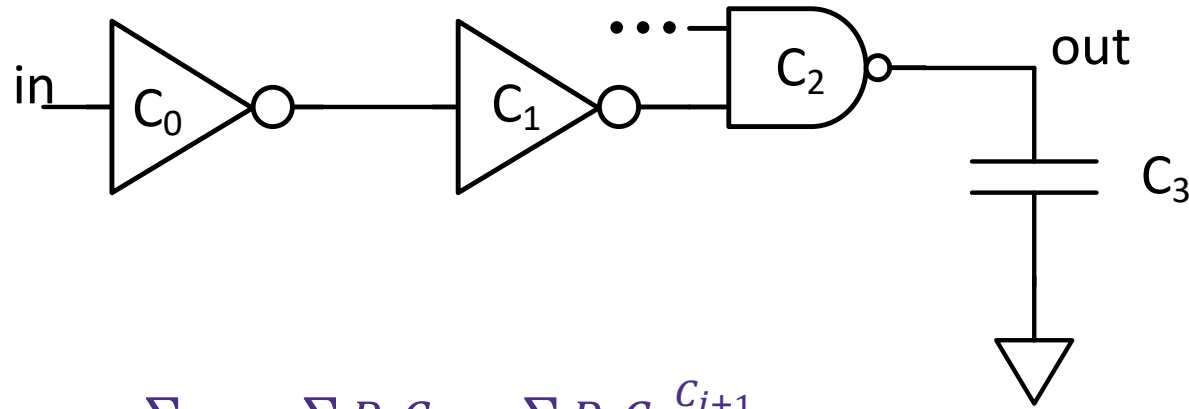
# Quick Note on General Sizing (Extra...)



 - $\tau = \sum \tau_i = \sum R_i C_{i+1} = \sum R_i C_i \frac{C_{i+1}}{C_i}$   
 $= \sum \tau_{intrinsic} \frac{C_{i+1}}{C_i}$
- $RC_{intrinsic,inv} = 3.5k_r k_c$
- $\tau_{intrinsic,nand} = 4.5k_r k_c$



 
# Quick Note on General Sizing (Extra...)




- $$\tau = \sum \tau_i = \sum R_i C_{i+1} = \sum R_i C_i \frac{C_{i+1}}{C_i}$$

$$= \sum \tau_{intrinsic} \frac{C_{i+1}}{C_i}$$
- $RC_{intrinsic,inv} = 3.5k_r k_c$
- $\tau_{intrinsic,nand} = 4.5k_r k_c$
- $$\tau = 3.5k_r k_c \frac{C_1}{C_0} + 3.5k_r k_c \frac{C_2}{C_1} + 4.5k_r k_c \frac{C_3}{C_2}$$
 
$$\tau_{inv\_units} = \frac{C_1}{C_0} + \frac{C_2}{C_1} + \frac{4.5}{3.5} \frac{C_3}{C_2}$$
- Rule-of-thumb: Maintain a stage-effort of  $\approx 3.4$


 
# Quick Note on General Sizing (Extra...)




- $$\tau = \sum \tau_i = \sum R_i C_{i+1} = \sum R_i C_i \frac{C_{i+1}}{C_i}$$


$$= \sum \tau_{intrinsic} \frac{C_{i+1}}{C_i}$$
- $RC_{intrinsic,inv} = 3.5k_r k_c$
- $\tau_{intrinsic,nand} = 4.5k_r k_c$
- $$\tau = 3.5k_r k_c \frac{C_1}{C_0} + 3.5k_r k_c \frac{C_2}{C_1} + 4.5k_r k_c \frac{C_3}{C_2}$$

$$\tau_{inv\_units} = \frac{C_1}{C_0} + \frac{C_2}{C_1} + \frac{4.5}{3.5} \frac{C_3}{C_2}$$

 Logical Effort
- Rule-of-thumb: Maintain a stage-effort of  $\approx 3.4$



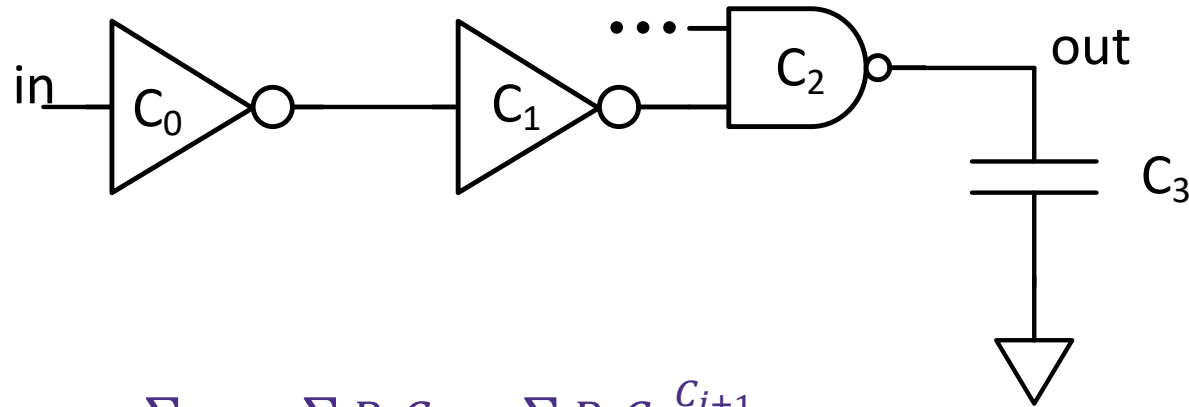
# Quick Note on General Sizing (Extra...)



- $$\tau = \sum \tau_i = \sum R_i C_{i+1} = \sum R_i C_i \frac{C_{i+1}}{C_i}$$

$$= \sum \tau_{intrinsic} \frac{C_{i+1}}{C_i}$$
- $RC_{intrinsic,inv} = 3.5k_r k_c$
- $\tau_{intrinsic,nand} = 4.5k_r k_c$
- $$\tau = 3.5k_r k_c \frac{C_1}{C_0} + 3.5k_r k_c \frac{C_2}{C_1} + 4.5k_r k_c \frac{C_3}{C_2}$$
 
$$\tau_{inv\_units} = \frac{C_1}{C_0} + \frac{C_2}{C_1} + \boxed{\frac{4.5}{3.5} \frac{C_3}{C_2}} \leftarrow \text{Stage Effort}$$
- Rule-of-thumb: Maintain a stage-effort of  $\approx 3.4$



# STATIC TIMING ANALYSIS

---