

Lecture 13: Memory Structures

*Based on material prepared by prof. Visvesh S.
Sathe*

Acknowledgements

All class materials (lectures, assignments, etc.) based on material prepared by Prof. Visvesh S. Sathe, and reproduced with his permission



Visvesh S. Sathe
Associate Professor
Georgia Institute of
Technology

<https://psylab.ece.gatech.edu>


UW (2013-2022)
GaTech (2022-present)

Memory Structures




- Dominant source of Tx count, area in many modern CMOS systems
- Increasingly key to system performance
 - On-chip: Register files, Cache memory
 - Off-chip : Main memory storage (DDR), Solid-state drives
- Key properties
 - Density (bits per mm²)
 - Latency (e.g. cycles to access)
 - Bandwidth

Memory Structures

 


- Dominant source of Tx count, area in many modern CMOS systems
- Increasingly key to system performance
 - On-chip: Register files, Cache memory
 - Off-chip : Main memory storage (DDR), Solid-state drives
- Key properties
 - Density (bits per mm²)
 - Latency (e.g. cycles to access)
 - Bandwidth

Memory Hierarchy

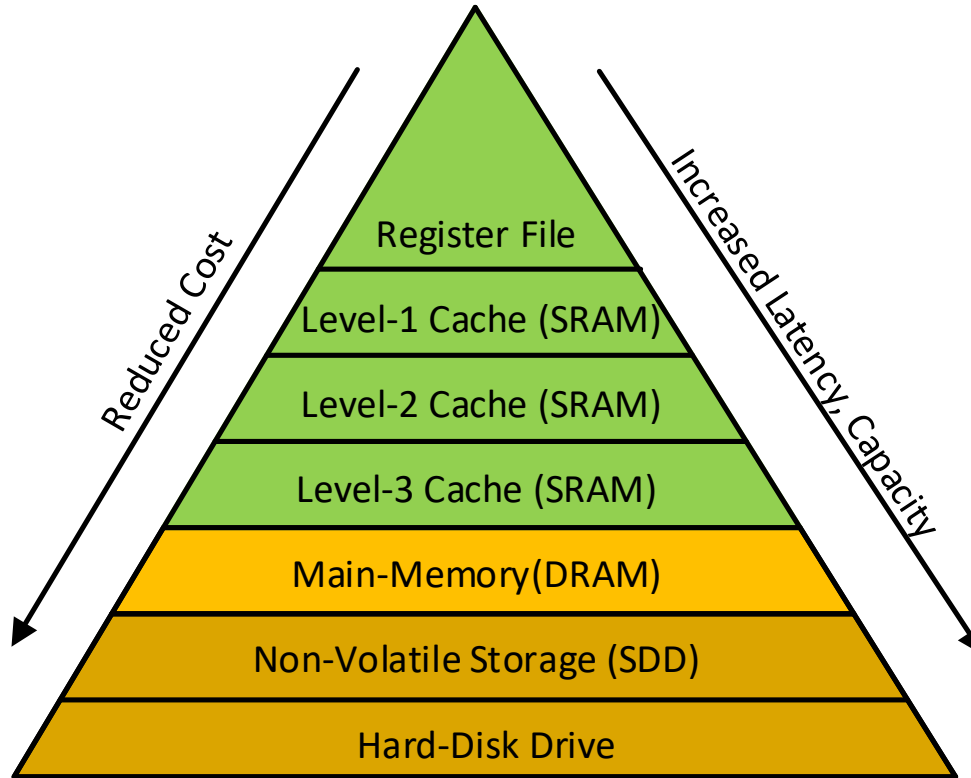

- Memory systems typically made up of *hierarchy* of different memory structures (cost, latency, bandwidth, capacity)
- Performance impact mitigated by
 - Locality of reference
 - Arithmetic intensity


We Will Cover...

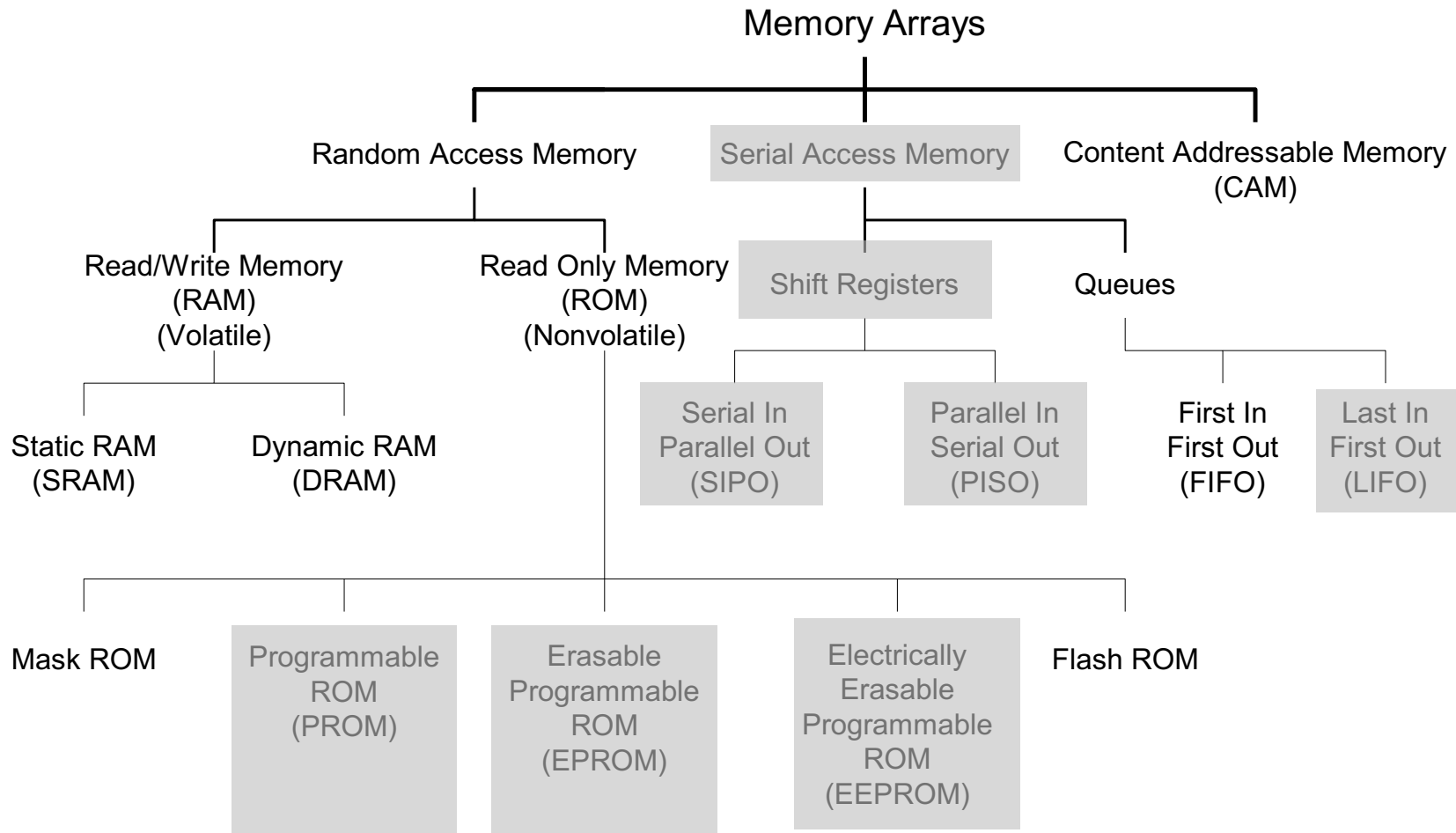

Source:W&H

Basic Random Access Memory Array Structure


 
- Random Access → Arbitrary data access order
- 2^n entry RAM
 - Query SRAM with n -bit address $A[n-1:0]$
 - Obtain 2^m bit data
 - 2MB memory with 64-bit data
 - $m=6$, $n=15$ (32000 rows!)
 - Folding yields improved aspect ratio



Source:W&H

Basic Random Access Memory Array Structure

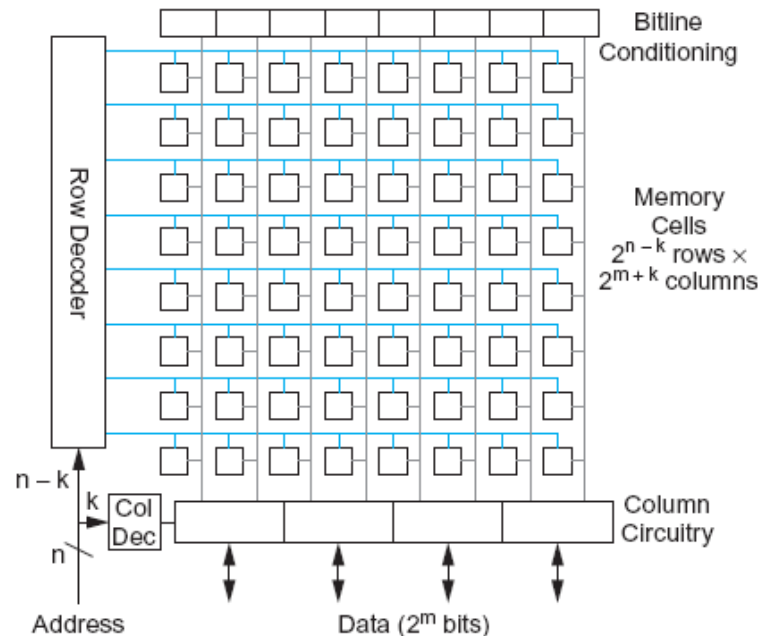
 
- Random Access → Arbitrary data access order
- 2^n entry RAM
 - Query SRAM with n -bit address $A[n-1:0]$
 - Obtain 2^m bit data
 - 2MB memory with 64-bit data
 - $m=6, n=15$ (32000 rows!)
 - Folding yields improved aspect ratio



Source:W&H

Basic Random Access Memory Array Structure

  - Random Access → Arbitrary data access order
- 2^n entry RAM
 - Query SRAM with n -bit address $A[n-1:0]$
 - Obtain 2^m bit data
 - 2MB memory with 64-bit data
 - $m=6, n=15$ (32000 rows!)
 - Folding yields improved aspect ratio




Additional notation

- Bitcell
- Ports



Source:W&H

Bitcell: Structure

 

- Area matters!! (Bitcell replicated $>10^6$ times)
- Wordline turns-on access transistors (only NMOS to save area)
- Back-to-back inverter structures enable static data storage
- Bitline is highly capacitive (wire-load, bit-cell loading)
 - Driving bitline to 1 is difficult, area consuming
 - Pre-charge the bitline to V_{dd} , bitline only responsible for pulldown
 - Read circuits in large memory structures don't wait for bitline to reach rails*
 - Need for dual-rail bitlines (Differential vs. single-ended sensing)



Operation (Read)

  

- Successful Read

- Precharge bit-lines to V_{dd}
- Activate word-line (turn on access transistors)
- Voltage divider with A_1 , D_1 as Q pulls *bit* low*, experiences voltage rise
- Q_b , *bit_b* polarities match (*bit_b* weakly helps stabilize Q_b)
- Q pulled down to gnd through D_1



Operation (Read)

  

- Successful Read

- Precharge bit-lines to V_{dd}
- Activate word-line (turn on access transistors)
- Voltage divider with A_1 , D_1 as Q pulls *bit* low*, experiences voltage rise
- Q_b , *bit_b* polarities match (*bit_b* weakly helps stabilize Q_b)
- Q pulled down to gnd through D_1

Operation (Read)

  


- Successful Read

- Precharge bit-lines to V_{dd}
- Activate word-line (turn on access transistors)
- Voltage divider with A_1 , D_1 as Q pulls *bit* low*, experiences voltage rise
- Q_b , *bit_b* polarities match (*bit_b* weakly helps stabilize Q_b)
- Q pulled down to gnd through D_1



Array Read Timing

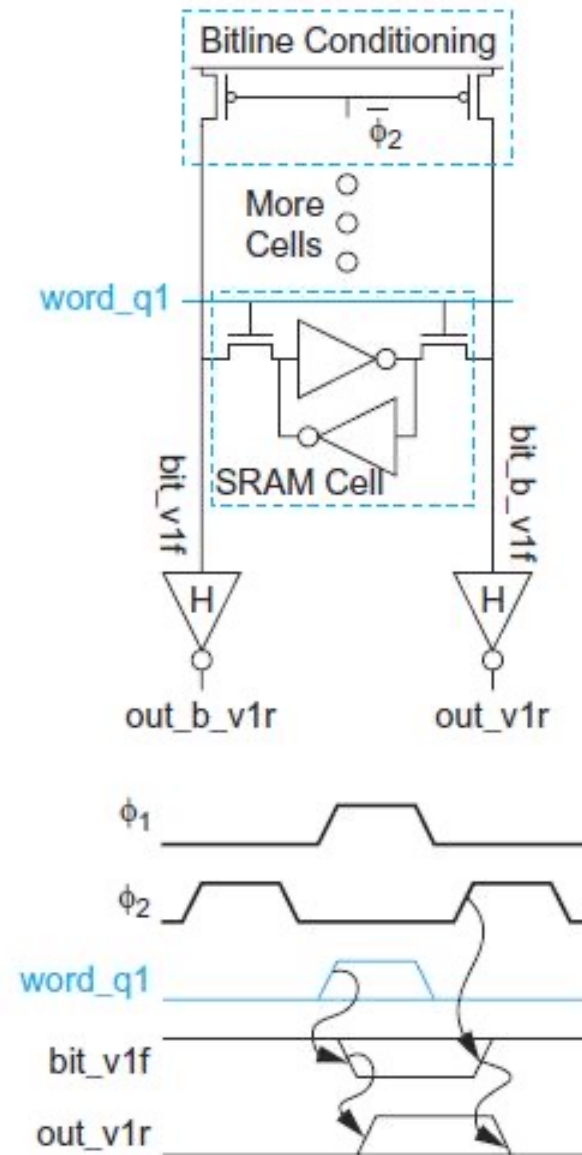- 2-stage process
 - 1st stage: precharge bitlines
 - 2nd stage: access bitcell
- *bit_v1f* does not have to go to 0
 - Differential read performed by sense-amplifiers



Source:W&H



Operation (Write)

  

- **Successful Write**

- bit , bit_b driven as per write-data
- Activate word-line (turn on access transistors)
- If stored data disagrees with write-data, fight ensues
 - Voltage divider arrangement between A_2 , U_2^* and A_1 , D_1^*
 - Q_b pulled toward gnd. \rightarrow U_1 and A_1 combine to overcome D_1 Q transitions upward
 - Positive feedback: Q Transition \rightarrow D_2 assists in pulldown, U_1 asserts pull-up



Operation (Write)

  

• Successful Write

- *bit*, *bit_b* driven as per write-data
- Activate word-line (turn on access transistors)
- If stored data disagrees with write-data, fight ensues
 - Voltage divider arrangement between A_2 , U_2^* and A_1, D_1^*
 - Q_b pulled toward gnd. $\rightarrow U_1$ and A_1 combine to overcome D_1 Q transitions upward
 - Positive feedback: Q Transition $\rightarrow D_2$ assists in pulldown, U_1 asserts pull-up



Operation (Write)

  

• Successful Write

- bit , bit_b driven as per write-data
- Activate word-line (turn on access transistors)
- If stored data disagrees with write-data, fight ensues
 - Voltage divider arrangement between A_2 , U_2^* and A_1, D_1^*
 - Q_b pulled toward gnd. $\rightarrow U_1$ and A_1 combine to overcome D_1 Q transitions upward
 - Positive feedback: Q Transition $\rightarrow D_2$ assists in pulldown, U_1 asserts pull-up


Operation (Write)

  

• Successful Write



- *bit*, *bit_b* driven as per write-data
- Activate word-line (turn on access transistors)
- If stored data disagrees with write-data, fight ensues
 - Voltage divider arrangement between A₂, U₂^{*} and A₁, D₁^{*}
 - Q_b pulled toward gnd. → U₁ and A₁ combine to overcome D₁ Q transitions upward
 - Positive feedback: Q Transition → D₂ assists in pulldown, U₁ asserts pull-up

Stability

 


- Fight during read and write operation in a latch can result in destructive reads and incomplete write
 - Bitcell tradeoff between size and robustness (V_{\min})
 - Bitcell relative sizing in descending order?:
- Static Noise Margins are popular for stability analysis (**Exercise**)
 - V_{th} variations are significant source of instability (\rightarrow Static margin analysis)
 - DC representation and analysis of a transient phenomenon
 - Millions of cells, PVT variation over a broad area
 - Heavily statistical in nature

Stability

  



- Fight during read and write operation in a latch can result in destructive reads and incomplete write
 - Bitcell tradeoff between size and robustness (V_{\min})
 - Bitcell relative sizing in descending order?:
- Static Noise Margins are popular for stability analysis (**Exercise**)
 - V_{th} variations are significant source of instability (\rightarrow Static margin analysis)
 - DC representation and analysis of a transient phenomenon
 - Millions of cells, PVT variation over a broad area
 - Heavily statistical in nature

Decoder Design

 

- Selecting which row to access involves decoding the address
- Decoder design provides necessary functionality
- **Exercise:** Bubble-propagate to implement the decode efficiently
- Total Latency depends on decode, bitcell access, bitline read, column mux
- $WL<n-1:0>$ lines run along memory rows. **Need to match height!! (pitch-matching)**

Decoder Design


 
 


- Selecting which row to access involves decoding the address
- Decoder design provides necessary functionality
- **Exercise:** Bubble-propagate to implement the decode efficiently
- Total Latency depends on decode, bitcell access, bitline read, column mux
- $WL<n-1:0>$ lines run along memory rows. **Need to match height!! (pitch-matching)**

Tolerating Faults

- Large number of memory cells
- Very difficult to guarantee that every single cell will work
- Structure and functionality allow for error-correction
- Error Detection and Correction
 - Maintain required hamming distance between valid symbols
 - If d is the minimum hamming distance between symbols
 - Possible to detect up to $d-1$ errors
 - Possible to correct for $\text{floor}[(d-1)/2]$
- Basic Block Code Example (7,4 Hamming Code):
 - 5-bits of data stored as 4b1011
 - Store a byte of data: 7b101 x_3 1 x_1 x_0
 - $X_3 = X_6 \text{ XOR } X_5 \text{ XOR } X_4 = 1 \text{ XOR } 0 \text{ XOR } 1 = 0$
 - $X_1 = X_6 \text{ XOR } X_5 \text{ XOR } X_2 = 1 \text{ XOR } 0 \text{ XOR } 1 = 0$
 - $X_0 = X_6 \text{ XOR } X_4 \text{ XOR } X_2 = 1 \text{ XOR } 1 \text{ XOR } 1 = 1$
 - Store : 7b1010101

DRAM

   


Source:W&H

- **Dynamic RAM**


- Memory content stored as the charge on a capacitor (Refresh needed)
- Very high density (order of magnitude higher than SRAM)
 - Special processing needed (Trench Capacitors). *Typically* incompatible with CMOS
- Read Operation
 - Precharge bit-line to $V_{DD}/2$
 - Turn on access transistor
 - Detect small-signal transition on bitline, amplify **and regenerate** bitline to write-back data
- Write Operation: Drive bitline, enable access transistor, charge/discharge node

DRAM Array

 - Many bitcells hanging off single bitline
 - Bitline capacitance \gg bitcell capacitance
- Sense amplifier detects if bitline moves \uparrow or \downarrow below $V_{dd}/2$
 - Use “control” bitline for differential sensing
 - Enables breaking up the bitline (mitigate bitline capacitance)





Mask ROMs

 

NOR-ROM



- Most compact on-chip memory storage
 - Microcode in processors
 - Signal processing (FIR Filters, FFT coefficients)
- 2-variants
 - Pseudo-nMOS logic based NOR gates
 - Pseudo-nMOS NAND ROM

NOR ROMs

 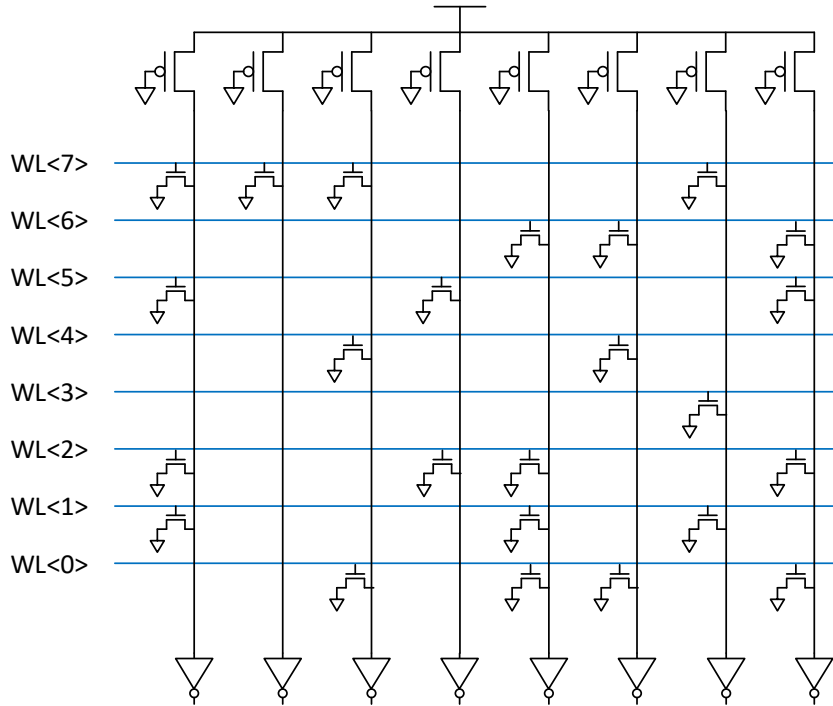



- Pseudo-nMOS NOR implementation (Avoid long, slow pullup)
 - Parallel NMOS connections
 - No full-rail swing
- For a given wordline, connect tx to bitline if corresponding bit is 1
 - Selection of wordline (active-high) pulls down bit-line, transitions output to 1

NAND ROMs

 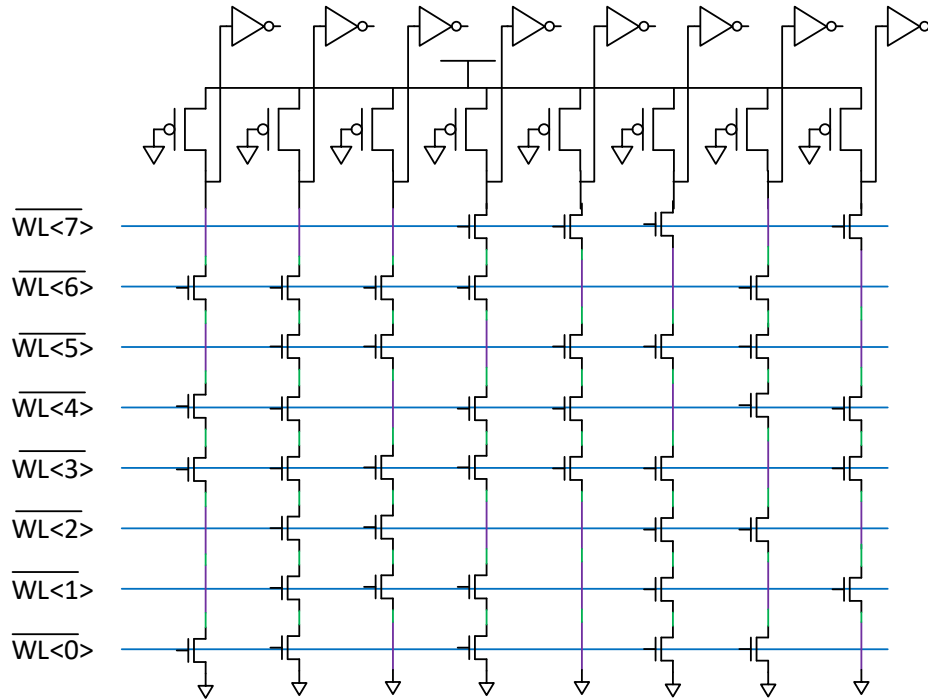

- Pseudo-nMOS NAND implementation
 - Series nMOS devices (Slower than NOR)
 - No full-rail swing
- Decode lines are active-low: All but selected WLs are 1
 - If transistor is present, $WL=0 \rightarrow$ BL remains high, output is low
 - If transistor not present, metal connection, $WL=0 \rightarrow$ BL pulldown, output 1
 - Insert transistor where you want to program a 0

NAND ROMs

 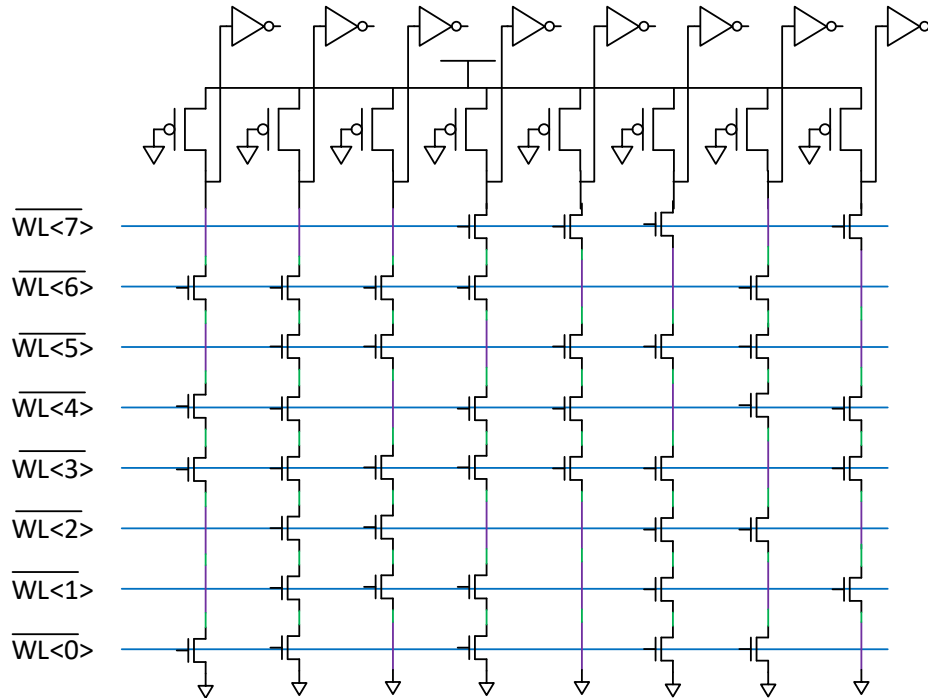

- Pseudo-nMOS NAND implementation

- Series nMOS devices (Slower than NOR)
- No full-rail swing


So..what's the benefit?




- Decode lines are active-low: All but selected WLs are 1

- If transistor is present, $WL=0 \rightarrow$ BL remains high, output is low
- If transistor not present, metal connection, $WL=0 \rightarrow$ BL pulldown, output 1
- Insert transistor where you want to program a 0

Layout Considerations

 

ROM Array

 


Array Decoder

Source:W&H



- ROM offers ~1 bit per transistor area, **very** compact
- Each bitcell is essentially 1 transistor high
 - Wordlines are spaced very close together
 - Decoder design needs some consideration (need to pitch match!)

Content Addressable Memory

 

- Extended SRAM
 - Capable of random read/write access into the array
 - “Content Addressable” capability. Match *data* query with content in memory and return row index (indices) that match to it
- Extensive usage in
 - Accelerators (Hashing)
 - Processors (Associative Cache Memory, TLB)
 - Routers

CAM Operation

  

- Random Read/Write similar to SRAM
- Matching operation
 - Pre-charge matchline to V_{dd}
 - Broadcast query on bitlines across the array
 - If a cell entry mismatches with a query, discharge matchline
 - Most (even all) matchlines discharge for each query (dissipative)
 - Matching lines are either priority encoded or combined for a single match/miss result
 - Segmented matching, NAND CAMs trade off speed for efficiency

Questions/Assignments

Reading

- Required W&H
 - SRAM 12.2.1-12.2.1.4
 - DRAM 12.3-12.3.1
 - ROM 12.4-12.4.2, 12.4.3
- Optional
 - SRAM 12.2.1.4 – 12.2.3, 12.2.5