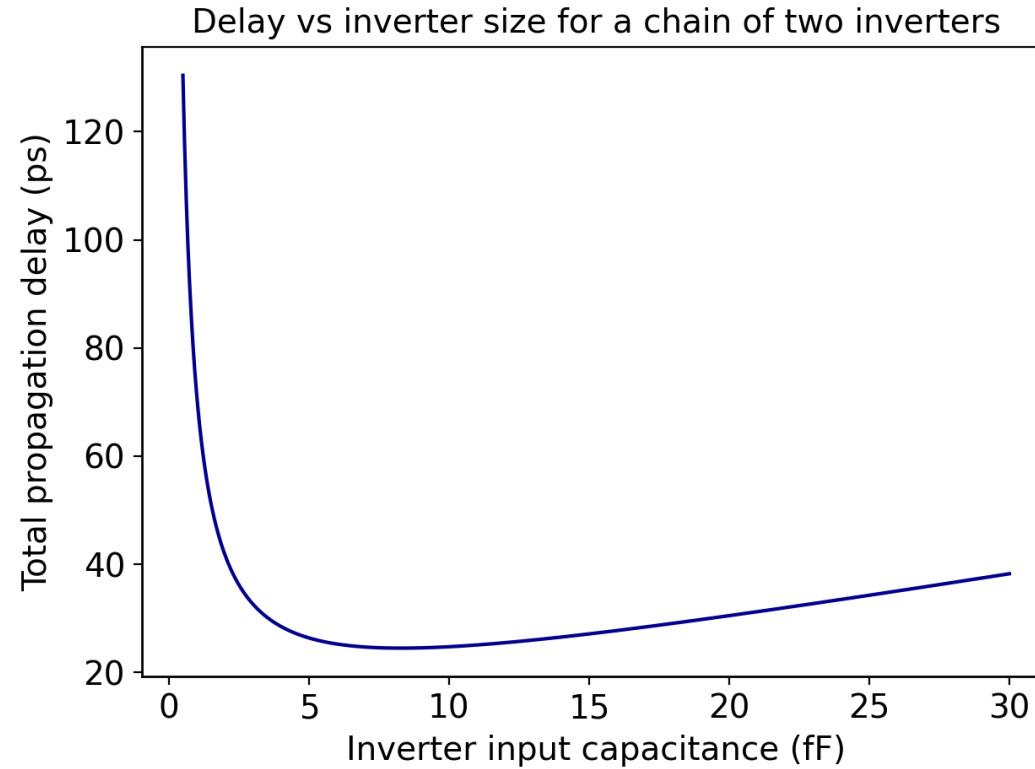



Practical sizing considerations



- Better to err on the side of larger drivers
- Min width issues (Allowed/Recommended for technology)
- Technique is great as an **initial starting point** for design


Optimal number of inverters
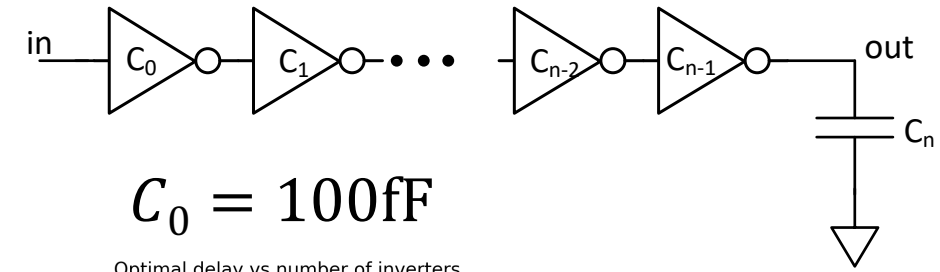
$$C_{in} = 2fF, \tau_{INV} = 3ps, p_d = 5ns$$




$$C_0 = 10fF$$

Optimal delay vs number of inverters

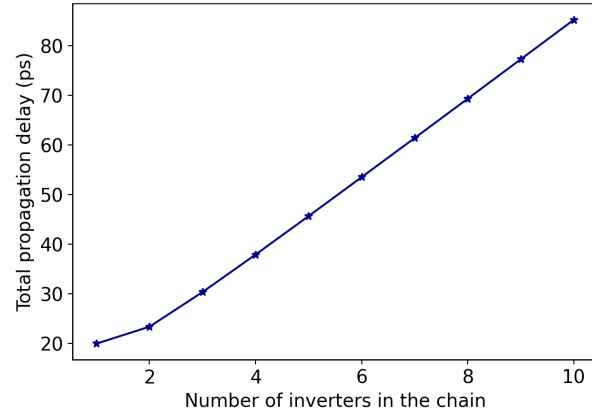


$$C_0 = 50fF$$

Optimal delay vs number of inverters

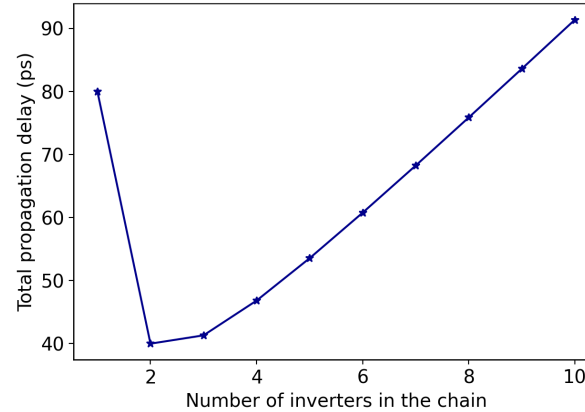


$$C_0 = 100fF$$

Optimal delay vs number of inverters

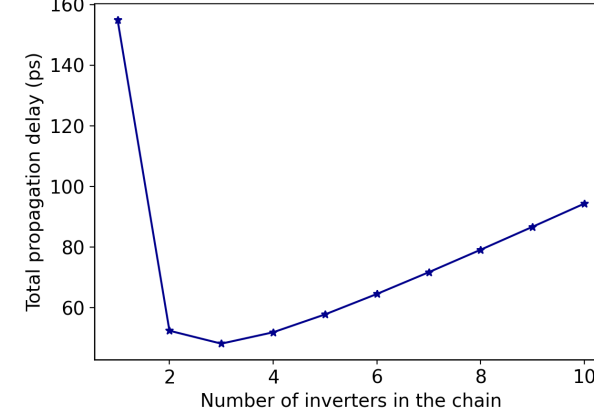


$$C_0 = 500fF$$

Optimal delay vs number of inverters

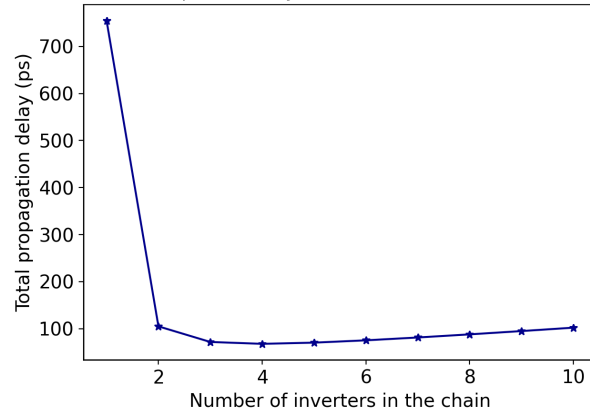

$$C_0 = 1000fF$$

Optimal delay vs number of inverters

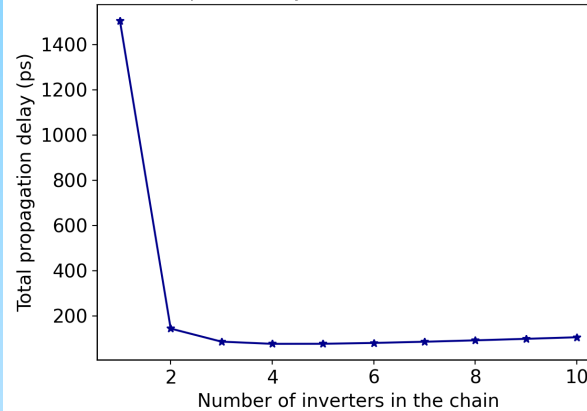

Optimal delay vs number of inverters

